

Laboratory 6 - Superposition and Thevenin Equivalent

Simulation

Problem 1

Superposition Theorem

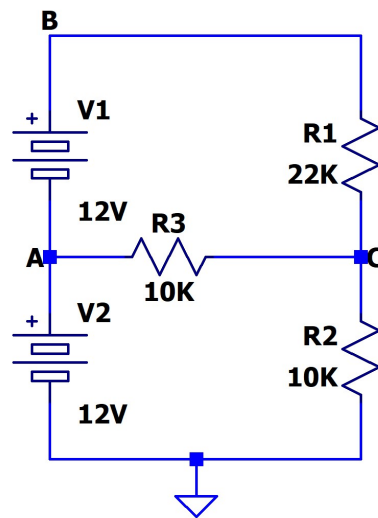


Fig 1. Circuit Diagram

--- Operating Point ---

| | | |
|---------|--------------|----------------|
| V(c) : | 9.33333 | voltage |
| V(b) : | 24 | voltage |
| V(a) : | 12 | voltage |
| I(R3) : | 0.000266667 | device_current |
| I(R2) : | -0.000933333 | device_current |
| I(R1) : | -0.000666667 | device_current |
| I(V1) : | -0.000666667 | device_current |
| I(V2) : | -0.000933333 | device_current |

Fig 2. Operating Points

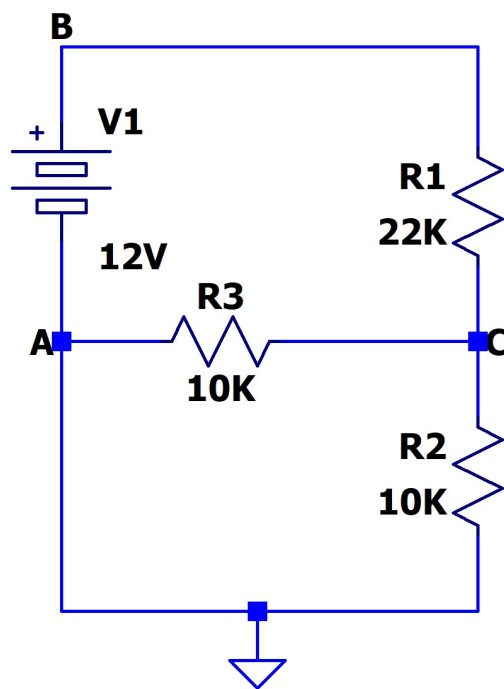
Superposition: Voltage Source V2 Short Circuited

Fig 3a. Circuit Diagram

--- Operating Point ---

| | | |
|----------|--------------|----------------|
| V(c) : | 2.22222 | voltage |
| V(b) : | 12 | voltage |
| I (R3) : | -0.000222222 | device_current |
| I (R2) : | -0.000222222 | device_current |
| I (R1) : | -0.000444444 | device_current |
| I (V1) : | -0.000444444 | device_current |

Fig 3b. Operating Points

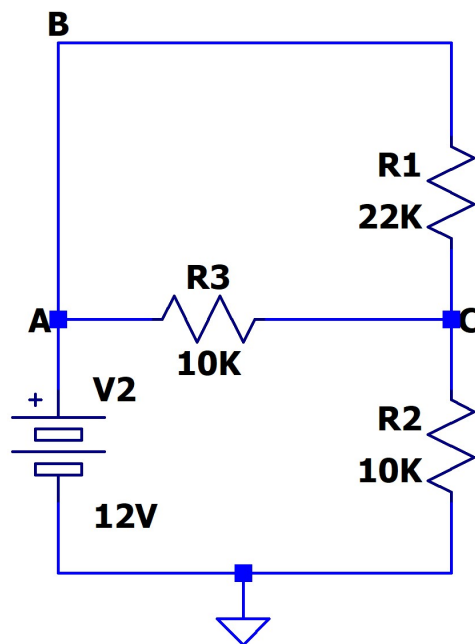
Superposition: Voltage Source V1 Short Circuited

Fig 4a. Circuit Diagram

--- Operating Point ---

| | | |
|---------|--------------|----------------|
| V(c) : | 7.11111 | voltage |
| V(a) : | 12 | voltage |
| I(R3) : | 0.000488889 | device_current |
| I(R2) : | -0.000711111 | device_current |
| I(R1) : | -0.000222222 | device_current |
| I(V2) : | -0.000711111 | device_current |

Fig 4b. Operating Points

Note that adding the voltages in Fig 3b and 4b. gives the same value as in Fig 2. Hence for a linear network superposition theorem is successfully proved.

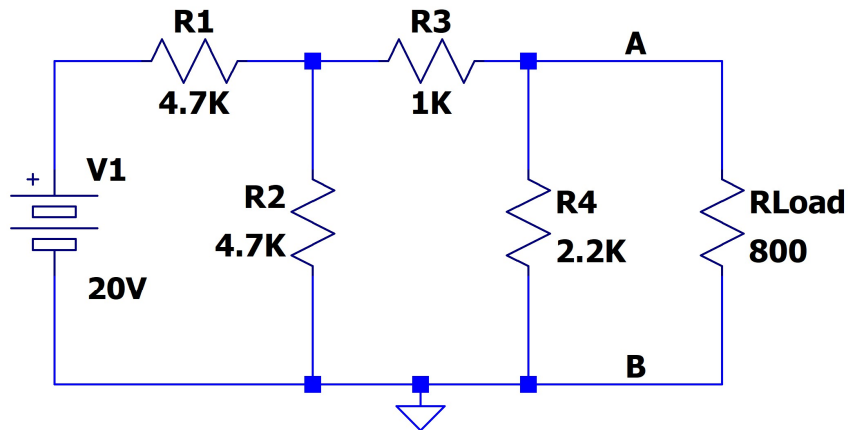
Problem 2**Thevenin Network Theorem**

Fig 5. Circuit Diagram

--- Operating Point ---

| | | |
|------------|--------------|----------------|
| V(n001) : | 20 | voltage |
| V(n002) : | 4.03048 | voltage |
| V(a) : | 1.49026 | voltage |
| I(Rload) : | 0.00186283 | device_current |
| I(R4) : | 0.000677392 | device_current |
| I(R3) : | 0.00254022 | device_current |
| I(R2) : | -0.000857549 | device_current |
| I(R1) : | -0.00339777 | device_current |
| I(V1) : | -0.00339777 | device_current |

Fig 6. Operating Points

Here V_A is the voltage across the load resistor R_L

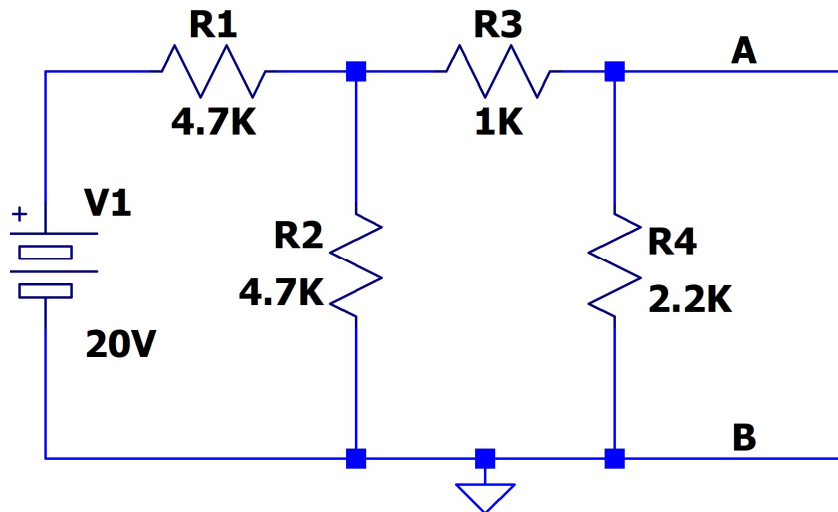
Problem 3**Thevenin Voltage (V_{TH})**

Fig 7. Circuit Diagram

--- Operating Point ---

| | | |
|------------|-------------|----------------|
| V (n001) : | 20 | voltage |
| V (n002) : | 5.76577 | voltage |
| V (a) : | 3.96396 | voltage |
| I (R4) : | 0.0018018 | device_current |
| I (R3) : | 0.0018018 | device_current |
| I (R2) : | -0.00122676 | device_current |
| I (R1) : | -0.00302856 | device_current |
| I (V1) : | -0.00302856 | device_current |

Fig 8. Operating Point

Here V_A is the Thevenin Voltage.

In analytical case the Thevenin voltage is calculated by setting sources to zero and connecting a 1V test voltage source at the output to find the resistance seen by the load.

Here R_{TH} is around 1.327 kOhms. This can be approximated as E32 series standard resistor of 1.3

kOhms.

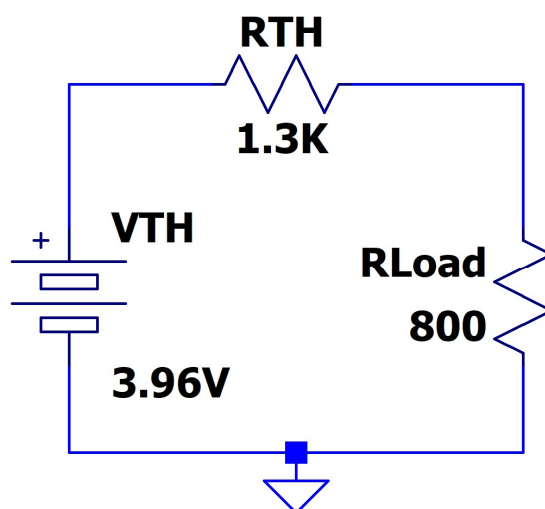
Problem 4**Thevenin Equivalent Model**

Fig 9. Circuit Diagram

--- Operating Point ---

| | | |
|------------|-------------|----------------|
| V(n002) : | 1.50857 | voltage |
| V(n001) : | 3.96 | voltage |
| I(Rload) : | -0.00188571 | device_current |
| I(Rth) : | -0.00188571 | device_current |
| I(Vth) : | -0.00188571 | device_current |

Fig 10. Operating Point

Here V_{N002} is the voltage across the load resistor which is same as the V_A of Fig 5 which is around 1.49026V. This difference is due to the assumption of standard E32 resistor series. Hence the Thevenin theorem is proved.

Error Percentage is around 0.667%

In case of LTSpice simulation the components are ideal and does not pose any resistance or parasitic capacitance. So, both the simulated value and calculated value will be the same.