

## Laboratory 6 - Superposition and Thevenin Equivalent

### Simulation

#### Problem 1

#### Superposition Theorem

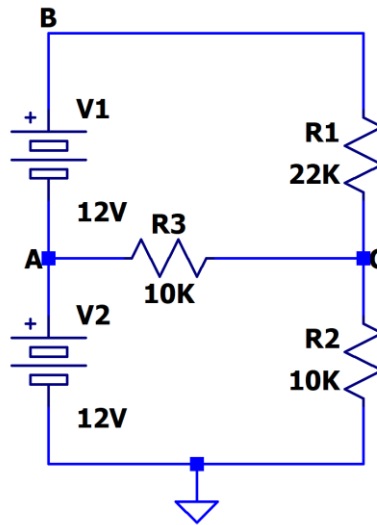


Fig 1. Circuit Diagram

--- Operating Point ---

V(c) :	9.33333	voltage
V(b) :	24	voltage
V(a) :	12	voltage
I (R3) :	0.000266667	device_current
I (R2) :	-0.000933333	device_current
I (R1) :	-0.000666667	device_current
I (V1) :	-0.000666667	device_current
I (V2) :	-0.000933333	device_current

Fig 2. Operating Points

Superposition: Voltage Source V2 Short Circuited

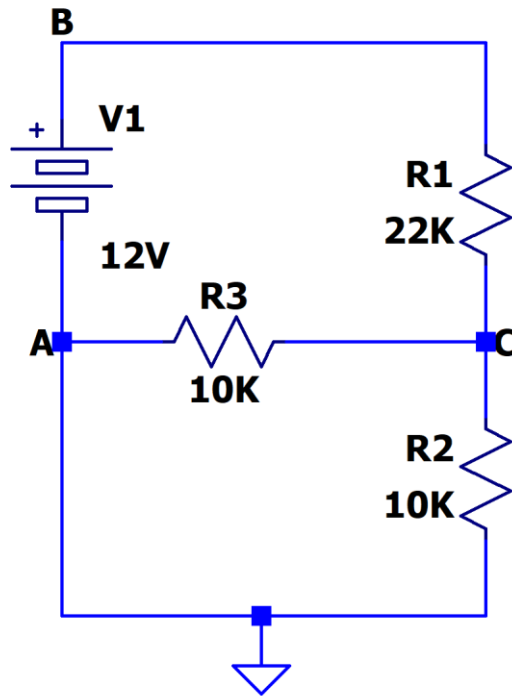


Fig 3a. Circuit Diagram

--- Operating Point ---

V(c) :	2.22222	voltage
V(b) :	12	voltage
I(R3) :	-0.000222222	device_current
I(R2) :	-0.000222222	device_current
I(R1) :	-0.000444444	device_current
I(V1) :	-0.000444444	device_current

Fig 3b. Operating Points

**Superposition: Voltage Source V1 Short Circuited**

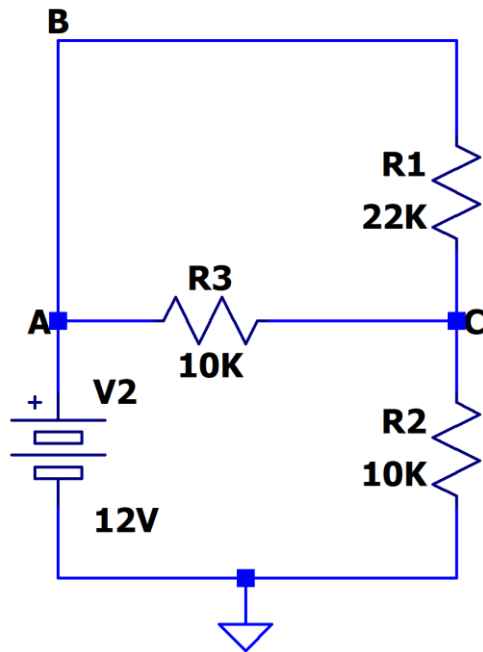


Fig 4a. Circuit Diagram

--- Operating Point ---

V(c) :	7.11111	voltage
V(a) :	12	voltage
I (R3) :	0.000488889	device_current
I (R2) :	-0.000711111	device_current
I (R1) :	-0.000222222	device_current
I (V2) :	-0.000711111	device_current

Fig 4b. Operating Points

Note that adding the voltages in Fig 3b and 4b. gives the same value as in Fig 2. Hence for a linear network superposition theorem is successfully proved.

**Problem 2**

### Thevenin Network Theorem

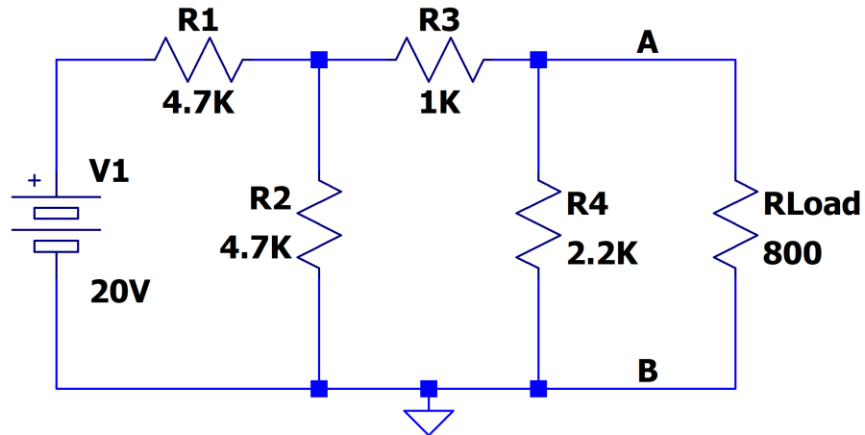


Fig 5. Circuit Diagram

--- Operating Point ---

V(n001) :	20	voltage
V(n002) :	4.03048	voltage
V(a) :	1.49026	voltage
I(Rload) :	0.00186283	device_current
I(R4) :	0.000677392	device_current
I(R3) :	0.00254022	device_current
I(R2) :	-0.000857549	device_current
I(R1) :	-0.00339777	device_current
I(V1) :	-0.00339777	device_current

Fig 6. Operating Points

Here  $V_A$  is the voltage across the load resistor  $R_L$

### Problem 3

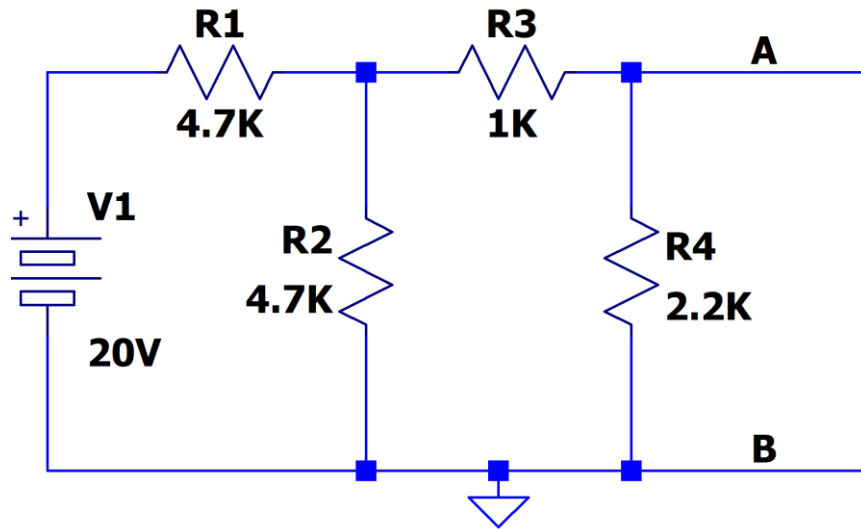
Thevenin Voltage ( $V_{TH}$ )

Fig 7. Circuit Diagram

## --- Operating Point ---

$V(n001) :$	20	voltage
$V(n002) :$	5.76577	voltage
$V(a) :$	3.96396	voltage
$I(R4) :$	0.0018018	device_current
$I(R3) :$	0.0018018	device_current
$I(R2) :$	-0.00122676	device_current
$I(R1) :$	-0.00302856	device_current
$I(V1) :$	-0.00302856	device_current

Fig 8. Operating Point

Here  $V_A$  is the Thevenin Voltage.

In analytical case the Thevenin voltage is calculated by setting sources to zero and connecting a 1V test voltage source at the output to find the resistance seen by the load.

Here  $R_{TH}$  is around 1.327 kOhms. This can be approximated as E32 series standard resistor of 1.3 kOhms.

### Problem 4

#### Thevenin Equivalent Model

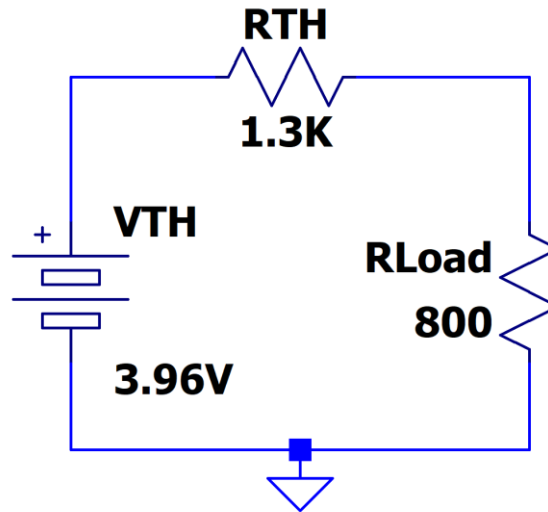


Fig 9. Circuit Diagram

--- Operating Point ---

V(n002) :	1.50857	voltage
V(n001) :	3.96	voltage
I(Rload) :	-0.00188571	device_current
I(Rth) :	-0.00188571	device_current
I(Vth) :	-0.00188571	device_current

Fig 10. Operating Point

Here  $V_{N002}$  is the voltage across the load resistor which is same as the  $V_A$  of Fig 5 which is around 1.49026V. This difference is due to the assumption of standard E32 resistor series. Hence the Thevenin theorem is proved.

Error Percentage is around 0.667%

In case of LTSpice simulation the components are ideal and does not pose any resistance or parasitic capacitance. So, both the simulated value and calculated value will be the same.