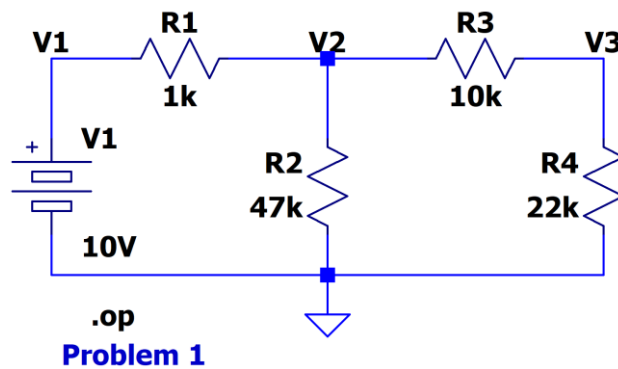


Laboratory-2 DC Power Supplies, Resistors and Digital Multi-Meters

SPICE Simulation


Problem 1



--- Operating Point ---

| | | |
|---------|--------------|----------------|
| V(v1) : | 10 | voltage |
| V(v2) : | 9.50095 | voltage |
| V(v3) : | 6.5319 | voltage |
| I(R4) : | -0.000296905 | device_current |
| I(R2) : | -0.000202148 | device_current |
| I(R3) : | -0.000296905 | device_current |
| I(R1) : | -0.000499052 | device_current |
| I(V1) : | -0.000499052 | device_current |

Fig 1. Circuit Diagram & Operating Points (LTSpice)

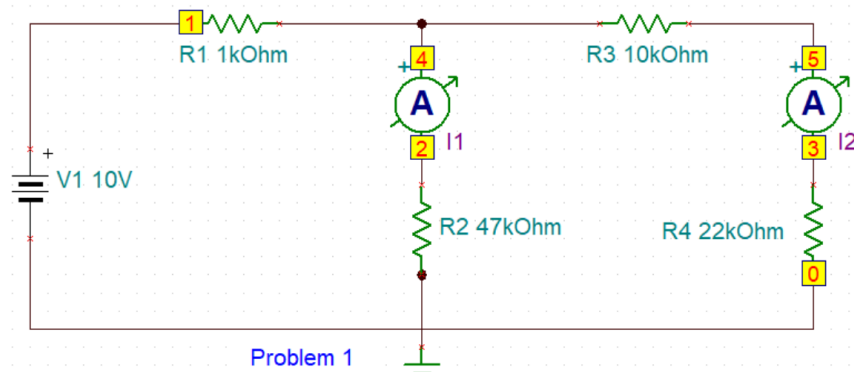

| | |
|-----------|----------|
| I_R1[1,4] | 499.05uA |
| I_R2[2,0] | 202.15uA |
| I_R3[5,4] | -296.9uA |
| I_R4[0,3] | -296.9uA |
| I1 | 202.15uA |
| I2 | 296.9uA |
| V_I1[4,2] | 0V |
| V_I2[5,3] | 0V |
| V_R1[1,4] | 499.05mV |
| V_R2[2,0] | 9.5V |
| V_R3[5,4] | -2.97V |
| V_R4[0,3] | -6.53V |
| V_V1[1,0] | 10V |
| VP_1 | 10V |
| VP_2 | 9.5V |
| VP_3 | 6.53V |
| VP_4 | 9.5V |
| VP_5 | 6.53V |

Fig 2. Circuit Diagram and Operating Point (TINA TI)

Table 1

| | Simulated Values |
|-----------------|---|
| V_{R1} | 499.05mV |
| V_{R2} | 9.5V |
| V_{R3} | -2.97V |
| V_{R4} | -6.53V |
| I_1 | 202.15uA |
| I_2 | 296.9uA |
| Power Delivered | $\approx 5\text{mW}$ |
| Power Absorbed | $1.92\text{mW} + 0.881\text{mW} + 1.94\text{mW} \approx 4.741\text{mW}$ |

Problem 2

1. What are the color codes for 1k, 10k and 20k resistors?

- a) 1k Brown Black Red
- b) 10k Brown Black Orange
- c) 20k Red Black Orange

2. What are the values of resistors with the following color codes (with units)?


- a) Red Red Yellow 22kOhms
- b) Brown Black Brown 100 Ohms
- c) Green Blue Violet 560MOhms

Maximum Possible Currents

- 3. What maximum current can a 1kOhm, 0.25W resistor can handle? 15.81 mA
- 4. What maximum current can a 47kOhm, 0.25W resistor can handle? 2.30 mA
- 5. What maximum current can a 10kOhm, 0.25W resistor can handle? 5 mA
- 6. What maximum current can a 22kOhm, 0.25W resistor can handle? 3.37 mA

Problem 3

Sweep the voltage source V1 from 0V to 5V with 0.5V increment and plot the curve of V1 versus I when voltage source V2 equals to 2.5V and 5V.

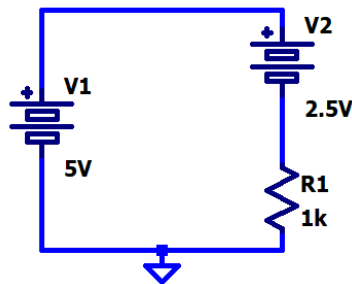

Problem 3 - Voltage-Current Characteristics

.dc V1 0 5 0.5

Fig 3. Circuit Diagram

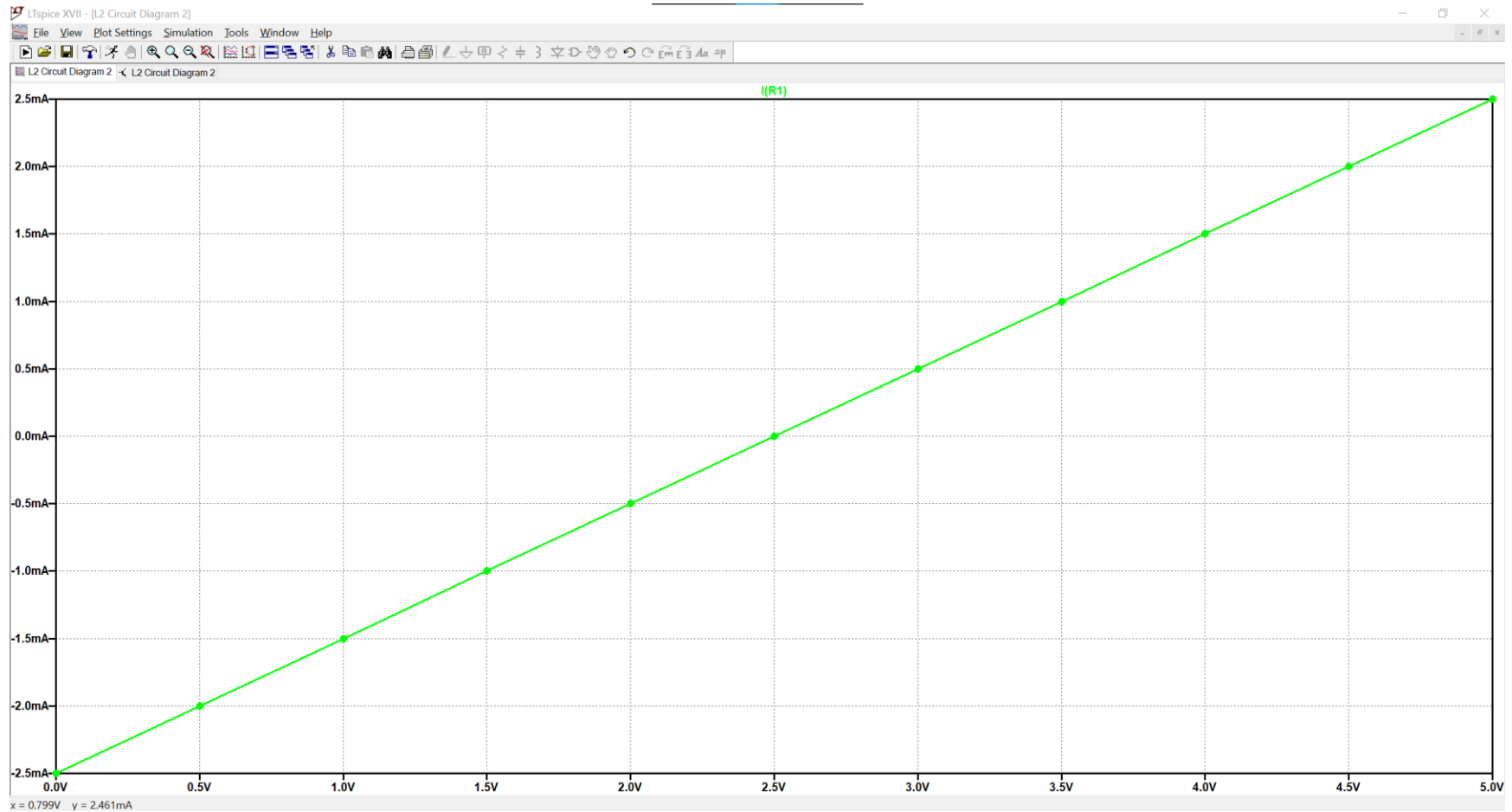


Fig 4a. Voltage Current Characteristics (Device Voltage 2.5V)

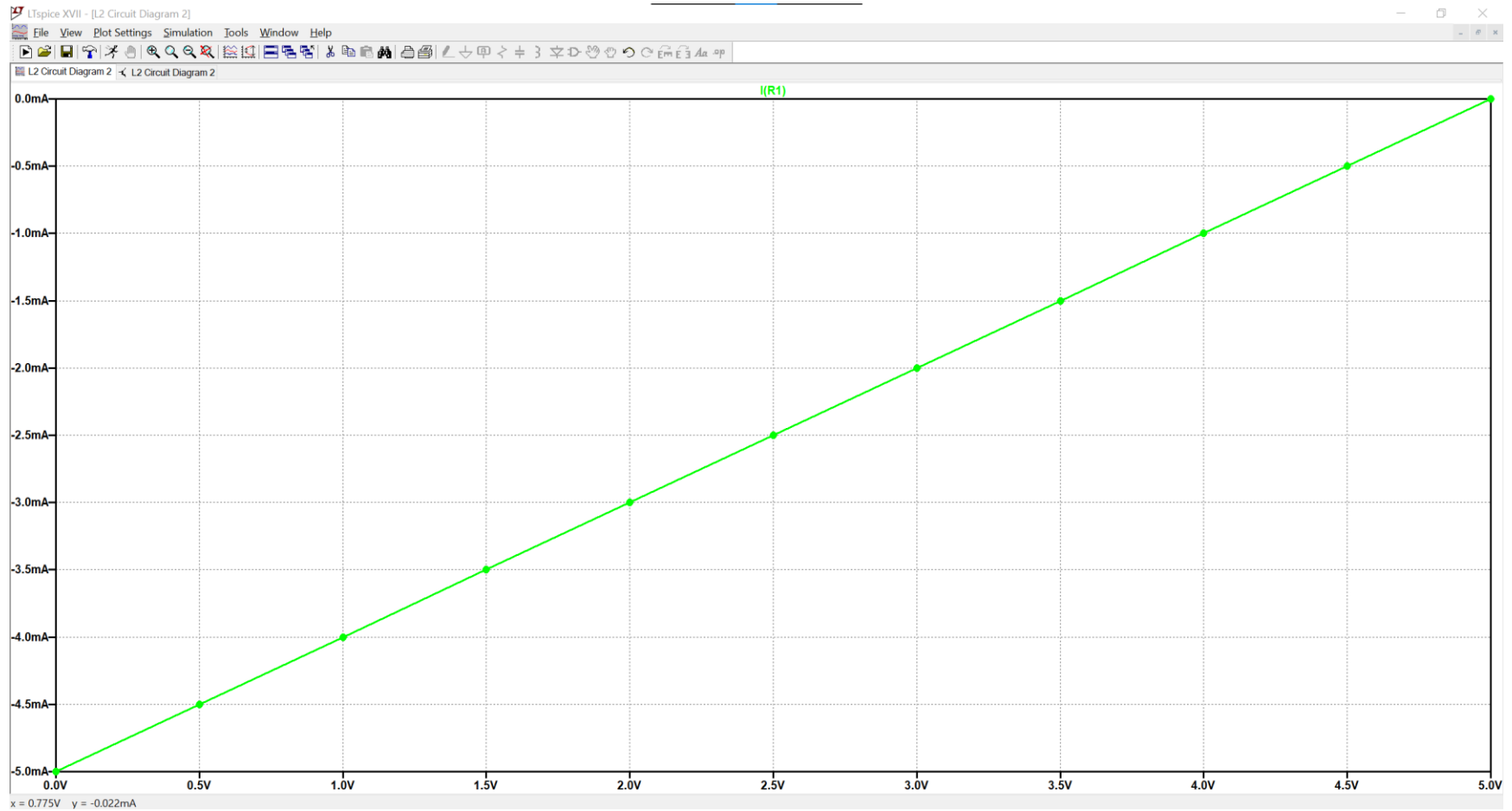


Fig 4b. Voltage Current Characteristics (Device Voltage 5V)

1. If the power rating for R1 is 0.25 W, what is the range to sweep when source voltage V2 equals to 2.5V and 5V?

$$V = \frac{P}{I} = \frac{0.25}{15.81 * 10^{-3}} = 15.81V$$

The maximum current through a 1kOhm resistor with a power rating of 0.25W is 15.81mA. So, when the V2 of device equals 2.5 and 5 volts, the input DC power supply can be swept upto 15V without any damage to the resistor.
